


Digital Logic Design Assignment 10 - EC2019-39

Chetan sarigala





December 16, 2020

1 EC2019 39

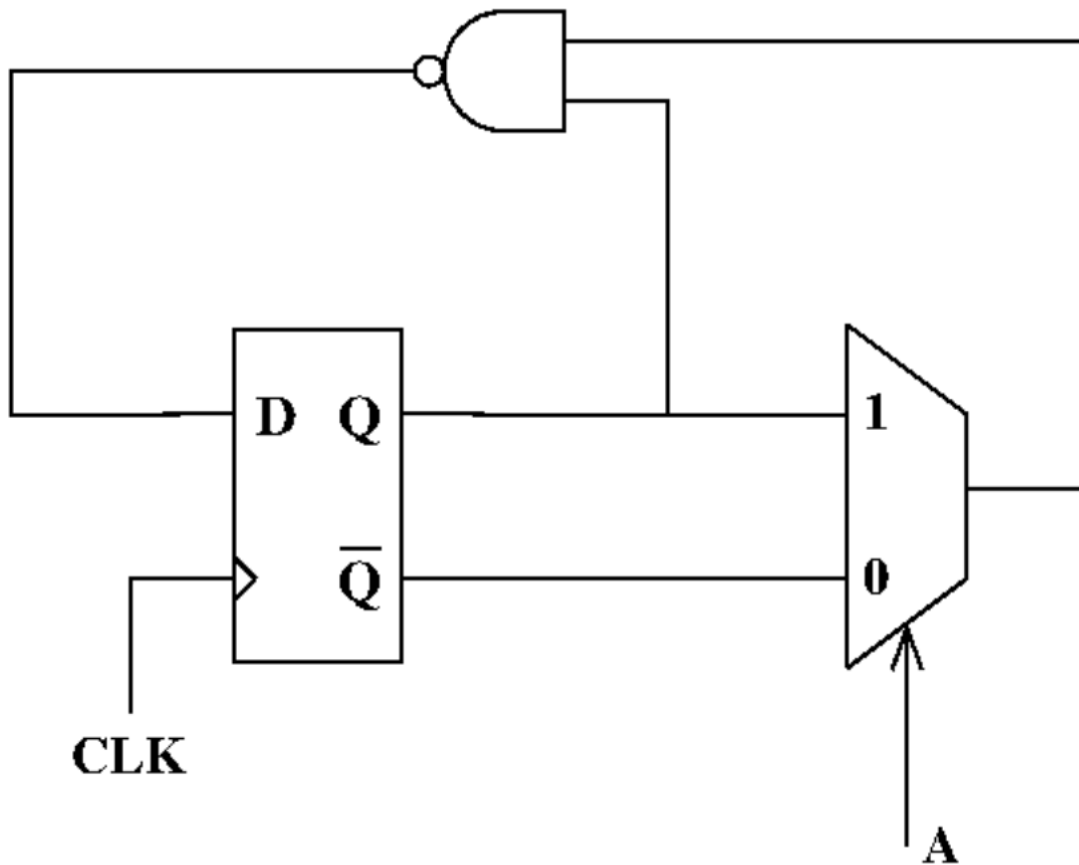The state transition diagram for the circuit is



    The following circuit (figure 1) has one D flip flop, one 2*1 multiplexer and one nand gate.



Now let us assume that output of the multiplexer as y.
if A=0 then the output y=1.

$$D = \overline{Q}.y.$$

$$D = \overline{Q} + \overline{y}.$$

the possible ways for output Q=0,1.

now let us assume that the output Q = 0 then $\overline{Q} = 1$.

then $D = 1 + 0$. $D = 1$.

when A = 1

then the output y = 0.

$$D = \overline{Q}.y.$$

$$D = 1.$$

Now let us take Q = 1.

then when A = 0, y = 1.

$$D = \overline{Q} + \overline{y}$$

$D = 0$
 Similarly,
 if $A = 1, y = 0$.
 then $D = \overline{Q \cdot y}$
 $D = 0 + 1$.
 $D = 1$.
 Therefore option (C) is correct.

