

Digital Logic Design Assignment 10 - EC2019-39

Chetan sarigala

December 16, 2020

1 EC2019 39

The state transition diagram for the circuit is

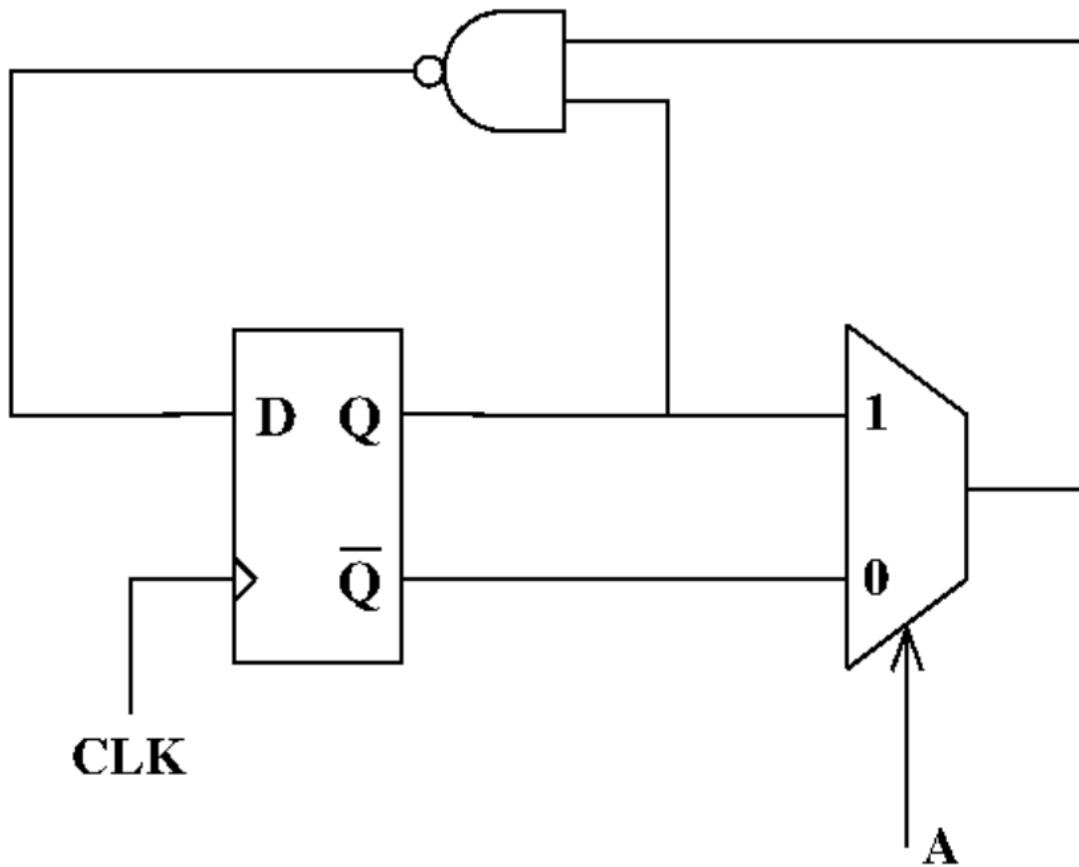


Figure 1

 


Figure 2

The following circuit (figure 1) has one D flip flop, one 2*1 multiplexer and one nand gate.

Now let us assume that output of the multiplexer as y .

if $A=0$ then the output $y=1$.

$$D = \overline{Q} \cdot y.$$

$$D = \overline{Q} + \overline{y}.$$

the possible ways for output $Q=0,1$.

now let us assume that the output $Q = 0$ then $\overline{Q} = 1$.

then $D = 1 + 0$. $D = 1$.

when $A = 1$

then the output $y = 0$.

$$\text{then } D = \overline{Q} \cdot y.$$

$D = 1$.
 Now let us take $Q = 1$.
 then when $A = 0$, $y = 1$.
 $D = \overline{Q} + \overline{y}$
 $D = 0$
 Similarly,
 if $A = 1$, $y = 0$.
 then $D = \overline{Q} \cdot y$
 $D = 0 + 1$.
 $D = 1$.
 Therefore option (C) is correct.

